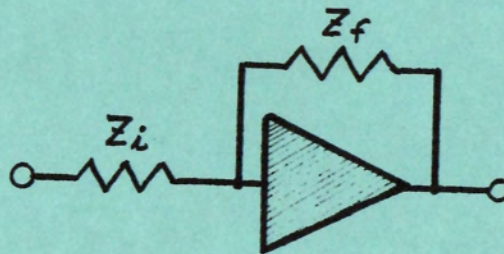


I N S T R U M E N T E N G I N E E R I N G
T E K T R O N I X , I N C .

N O T E S O N O P E R A T I O N A L A M P L I F I E R
A p p l i c a t i o n s



Hiro Moriyasu
January, 1962

Copyright © 1962 by Tektronix, Inc.,
Beaverton, Oregon. Printed in the United
States of America. All rights reserved. Con-
tents of this publication may not be repro-
duced in any form without permission of
the copyright owner.

TABLE OF CONTENTS

Basic Operation Amplification; Integration; Differentiation; Summation.	1
Voltage-Current Conversions Current of voltage; Voltage to current; Voltage to voltage; Current to current.	3
Gated Integrator Simple gating; Simple gating for (-) signal; Relay gating for low speed; Bridge gating.	4
Bandpass Amplifier Low pass amplifier; Band pass amplifier; Typical bandpass amplifier; Special purpose amplifier.	5
DC Measurements DC Slideback; DC slideback with large sig. compression.	6
High Input Impedance Amplifier Unity Gain Follower Amplifier; Non-inverting amplifier; High input impedance amplifier.	7
<u>NONLINEAR AMPLIFIERS</u>	
Diode Nonlinear Amplifier Simple nonlinear amplifier; Logarithmic type amplifier; Expansion amplifier.	8
Log Diode Nonlinear Amplifier Theoretical Logarithmic amplifier; Approximate logarithmic amplifier; Symmetrical nonlinear amplifier; Symmetrical nonlinear amplifier.	9
Transistor Nonlinear Amplifiers Approximate logarithmic; Symmetrical nonlinear amplifier; Symmetrical compressed amplifier; Possible nonlinearity control.	10
Vacuum Tube Nonlinear Amplifiers Square Root Amplifier; Root Function; Power function.	11
Zener Diode Nonlinear Amplifiers Limiter Amplifier; Squaring Amplifier; Compres- sion Amplifier; Expansion Amplifier. Dead zone; Back-lash; Relay	12 13
Absolute Value Amplifier Full-wave rectification; Fullwave rectification (low Level).	14

Table of contents continued

DIGITAL TECHNIQUES

Switching Amplifier (bistable)	15
Bistable comparator; Bistable comparator; Bistable Multivibrator;(single input); Bistable Multivibrator (two inputs).	
Digital Techniques	16
Pulse-height to Time Converter; Time to voltage converter; DC voltage to frequency converter; Binary to voltage converter.	
Peak Memory Amplifier	17
Peak Memory amplifier; Fast response peak memory amplifier; Integrator peak memory.	
Sample-Hold Amplifier	18
Sample-hold; Simple-hold amplifier.	
Sampled-Data	19
Sampling integration; Sampled-pulse integration; Sampled-pulse differentiation; Possible risetime compensation circuit.	

OTHER APPLICATIONS

L.F. Function Generators	20
Triangle, Square, Sawtooth & Pulse generator; L.F. Sine generator.	
CRT Function Generator	21
Simple System; Differential fast system; Mask cutting.	
Segments Function Generator	22
B-H Loop Plotting	23
B-H Curve plotting.	
Capacity Measurement	24
Basic idea; Capacity 1pf to 10uf Wide range capacity meter.	
Risetime Beam Intensifier	25
Risetime intensifier; Rise & fall time inten- sifier; Intensity control.	

Table of contents continued

Velocity Acceleration Studies 26
Velocity plot; Acceleration; Speed-Torque Plot.

Transfer Functions 27

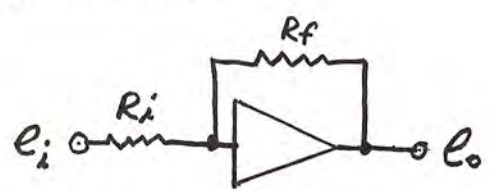
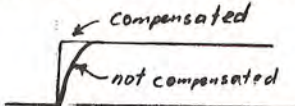
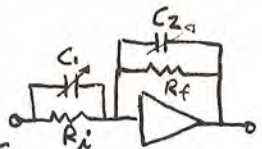
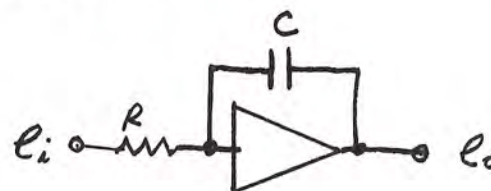

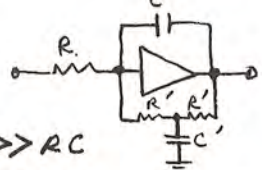
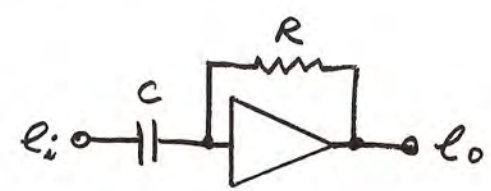
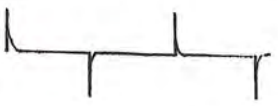
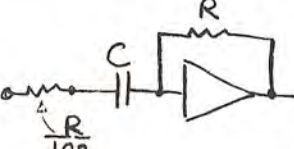
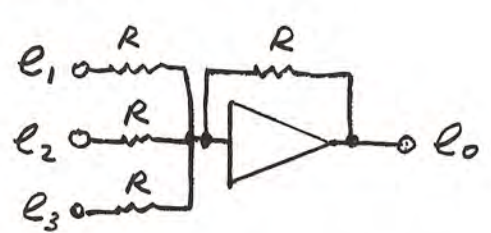
$$G(s) = -k; \quad G(s) = \frac{-k}{s}; \quad G(s) = -ks;$$


$$G(s) = \frac{-k}{(Ts - 1)}$$

Tunnel Diode Studies 28

Tunnel Diode stability; Tunnel diode E-I curve;
Tunnel diode di/de curve.


Tunnel diode switching; Block diagram; Analog
solution of risetime. 29

BASIC OPERATIONS	CHARACTERISTICS
<p>Amplification</p>  $e_o = -\frac{R_f}{R_i} e_i$	<p>Gain of the amplifier is determined by the ratio of R_f to R_i. note the negative sign.</p> <p>Step function response </p> <p>High frequency compensation  $R_i C_1 = R_f C_2$</p>
<p>Integration</p>  $e_o = -\frac{1}{RC} \int e_i dt$	<p>Gain = $-\frac{1}{RC 2\pi f}$</p> <p>Square wave response </p> <p>Drift compensation for ac integration  $R'C' \gg RC$</p>
<p>Differentiation</p>  $e_o = -RC \frac{de_i}{dt}$	<p>Gain = $-RC 2\pi f$</p> <p>Square wave response </p> <p>H.F. noise suppression for L.F. differentiation </p>
<p>Summation</p>  $e_o = -(e_1 + e_2 + e_3)$	<p>Gain of this summing amplifier is one. Higher gain can be obtained by increasing the feedback resistor just the same way as the amplifier. Here again output sign is negative.</p>

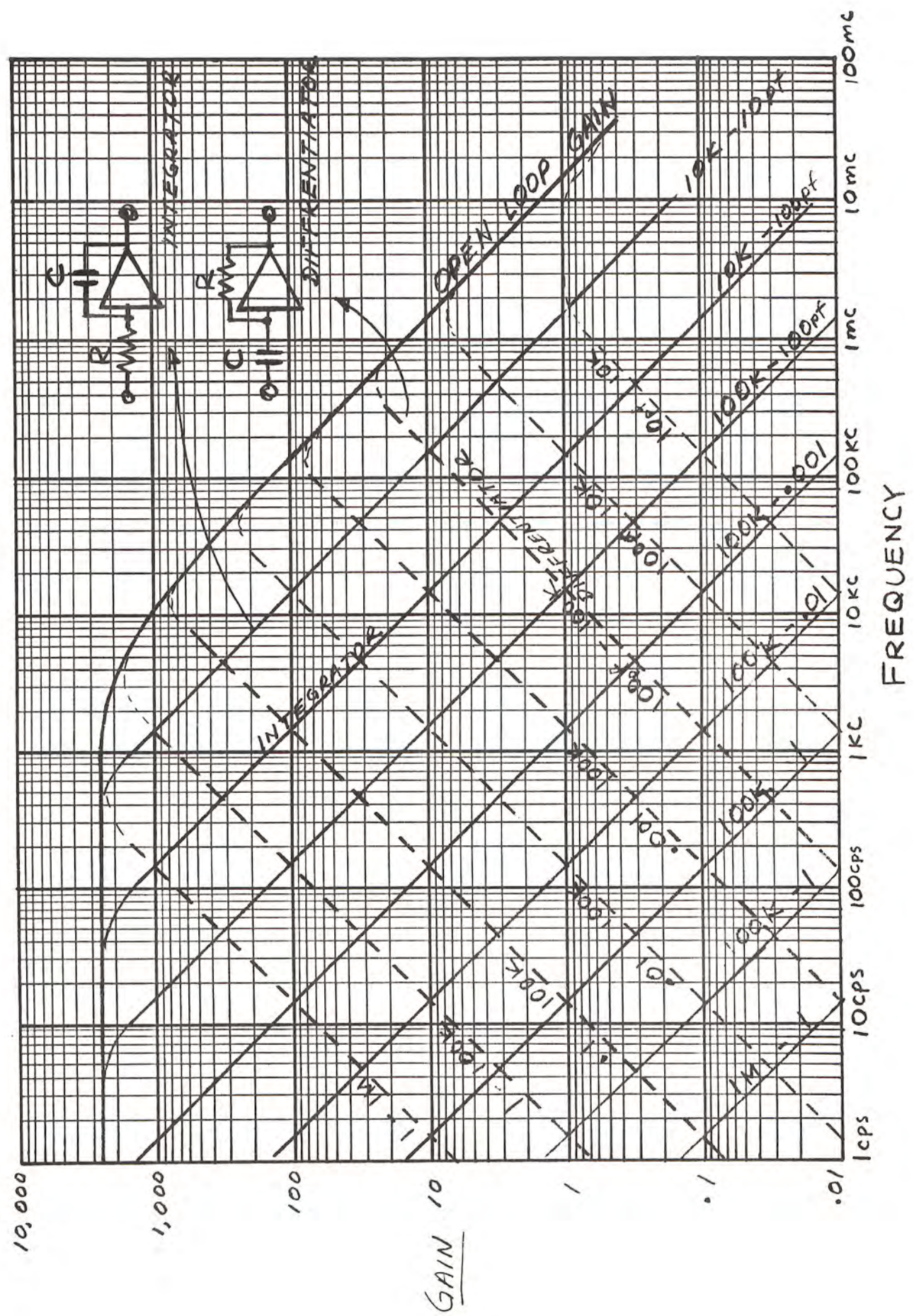

VOLTAGE - CURRENT CONVERSIONS


Current to voltage

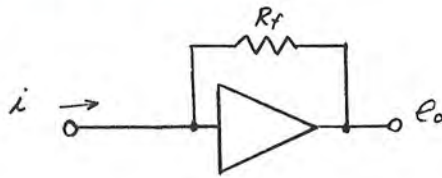


$$e_o = -i R_f$$

Very low current measurement application. The output voltage is proportional to the input current. For example $R_f = 1 \text{ meg}$ give 1 volt/ua .

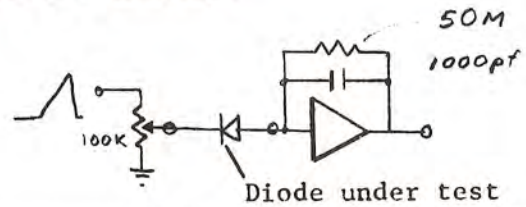Typical application: diode leakage test to 1 nanoamp .



Voltage to current

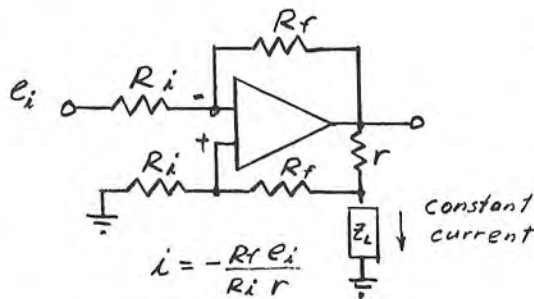


$$i = -\frac{R_f e_i}{R_i r}$$

Positive feedback to grid maintains voltage across r constant. If R_f and R_i are made much higher than load impedance, almost all the current flows into the load.

Then
$$i = \frac{-R_f e_i}{R_i r}$$

If
$$Z_L \ll R_f + R_i$$

Voltage to voltage

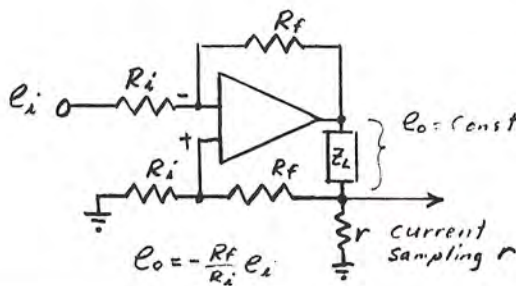


$$e_o = -\frac{R_f}{R_i} e_i$$

Amplifier maintains constant voltage across the load, while allowing insertion of current sampling resistor. This may be used to study nonlinear component testing, using scope sawtooth.

$$e_o = -\frac{R_f}{R_i} e_i$$

Current to current







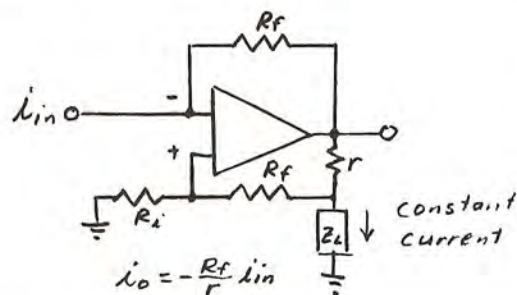


$$i_o = -\frac{R_f}{r} i_{in}$$

Current to current amplifier. The maximum output current is limited by the amplifier capability.


$$i_o = -\frac{R_f}{r} i_{in}$$

if
$$Z_L \ll R_f + R_i$$

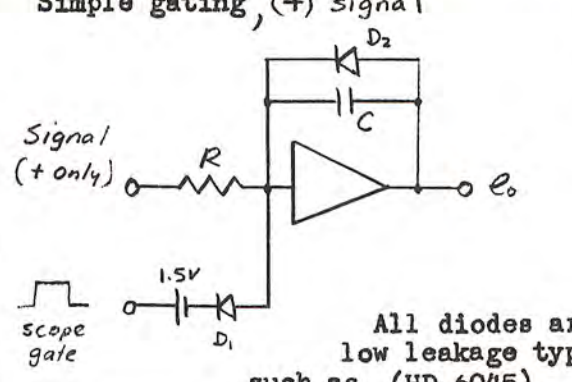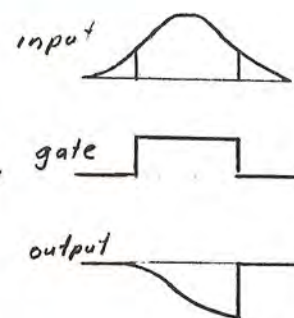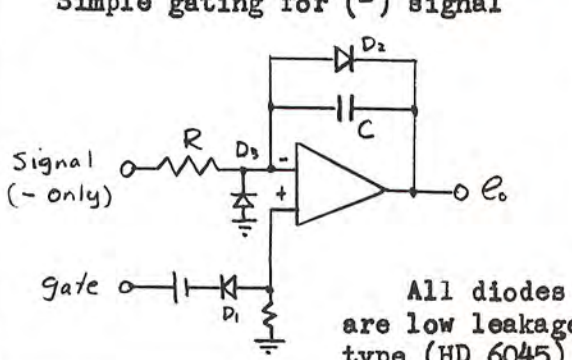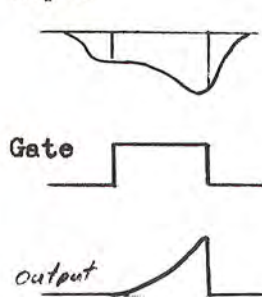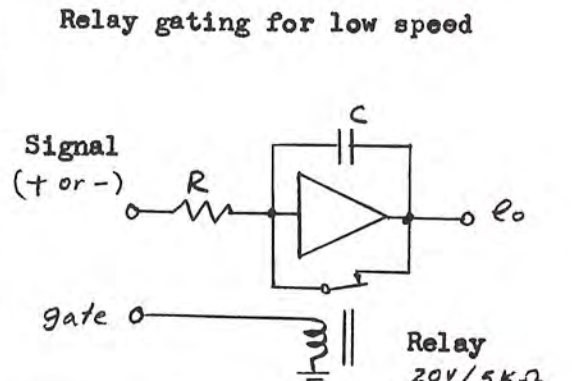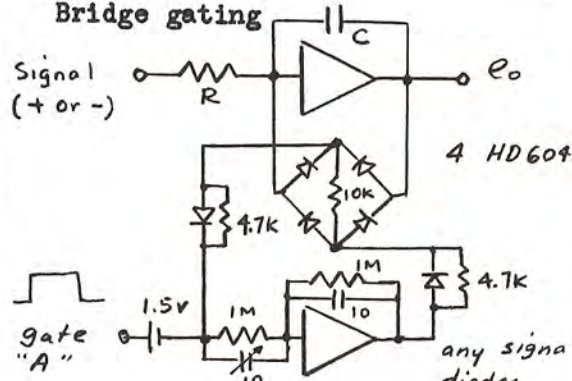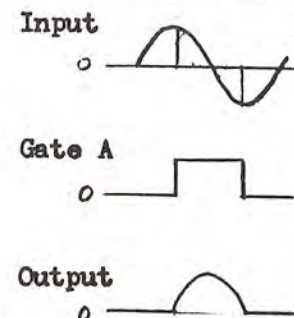
<p style="text-align: center;">GATED INTEGRATOR</p>	
<p>Simple gating, (+) signal</p>  <p style="text-align: right;">All diodes are low leakage type such as (HD 6045)</p>	<p>Gating integrator accepts positive signals only. When gate is zero output is clamped by D_2 to approx. +0.5V</p> 
<p>Simple gating for (-) signal</p>  <p style="text-align: right;">All diodes are low leakage type (HD 6045)</p>	<p>Negative signal can be gated by rearranging the circuit. The gate will drive grid. When gate is zero output is clamped to approx. -0.5V</p> 
<p>Relay gating for low speed</p>  <p style="text-align: right;">Relay 20V/5KΩ</p>	<p>For very slow speed application, relay can serve simple gating. Input can be + or -</p>
<p>Bridge gating</p>  <p style="text-align: right;">4 HD6045 any signal diodes</p>	<p>This arrangement uses diode bridge and gating amplifier B. It can accept + or - input signal. Output signal should not exceed the gating voltage. Using 535,45, "A" gate, any portion of curve may be integrated.</p> 

BANDPASS AMPLIFIER

Low pass amplifier

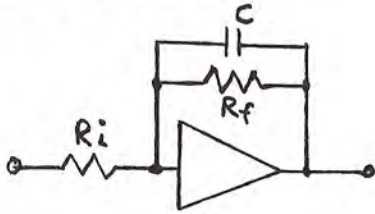


$$\text{Gain} = -\frac{R_f}{R_i}$$

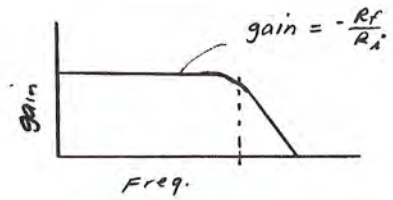


High Freq. response

$$f_{H.F.} = \frac{1}{2\pi R_f C} \text{ cps}$$

Band pass amplifier

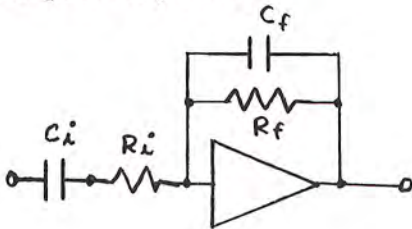

$$\text{Gain} = -\frac{R_f}{R_i}$$

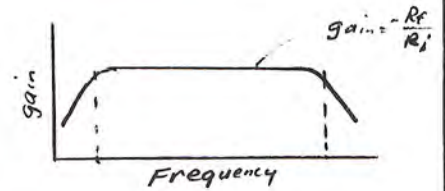


L.F. response

$$f_{L.F.} = \frac{1}{2\pi R_i C_i} \text{ cps}$$


H.F. response

$$f_{H.F.} = \frac{1}{2\pi R_f C_f} \text{ cps}$$

Typical bandpass amplifier


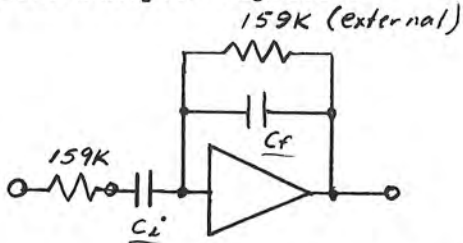


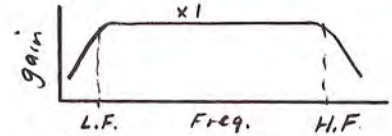C_i and C_f selected by switch 10pf - 1ufd



L.F.	C_i	H.F.	C_f
1cps	1ufd	100KC	10pf
10c	.1	10KC	.0001ufd
100c	.01	1KC	.001
1KC	.001	100c	.01
10 KC	.0001	10c	.1
100KC	10pf	1c	1ufd





Special purpose amplifier

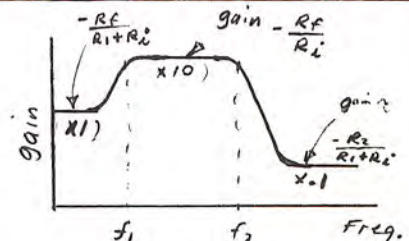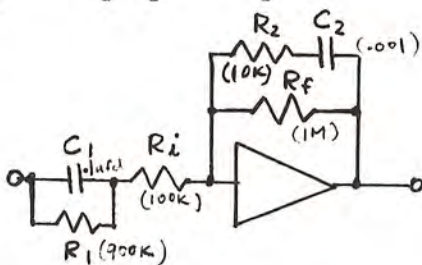

$$f_1 = \frac{1}{2\pi R_i C_1} \text{ cps} \quad (159\text{cps})$$


$$f_2 = \frac{1}{2\pi R_f C_2} \text{ cps} \quad (159\text{cps})$$

DC MEASUREMENTS

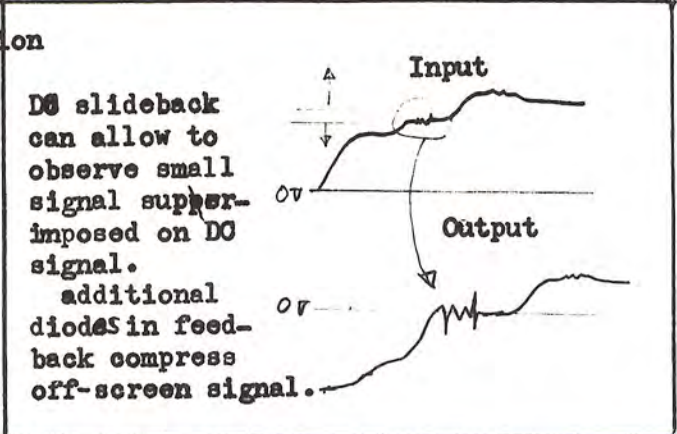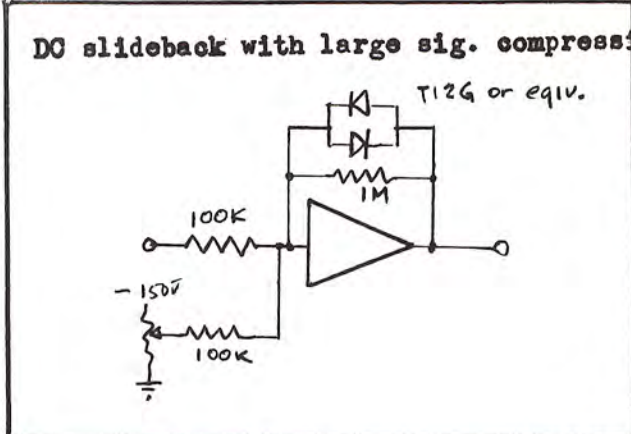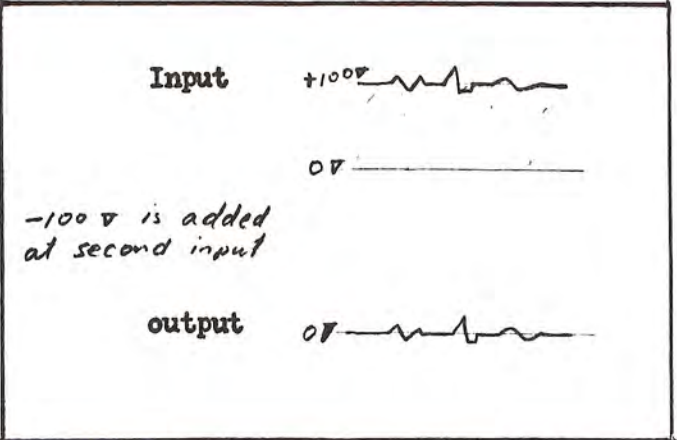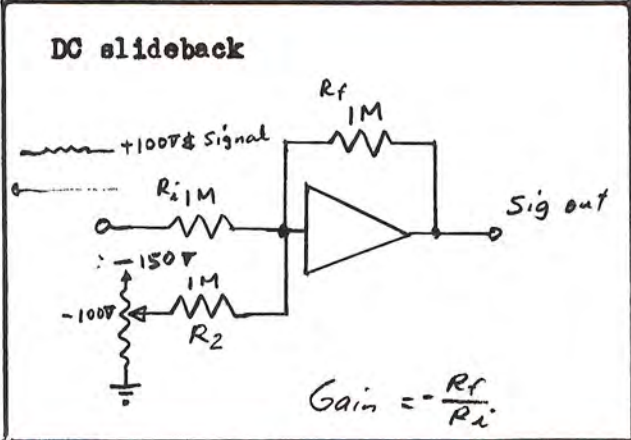

HIGH INPUT IMPEDANCE AMPLIFIER

Unity Gain Follower Amplifier

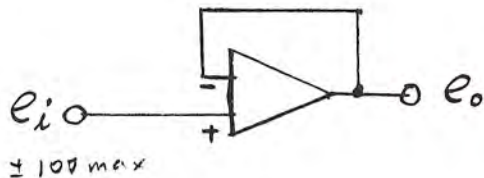

$$e_o = e_i$$


Input grid current is very low, typically less than .3 namp thus equivalent input impedance may be expressed

$$R = \frac{e}{i}$$

For 1 volt input voltage

$$R = \frac{1 \text{ v}}{3 \times 10^{-10}} = 3.3 \text{ meg equiv}$$


Non-inverting amplifier

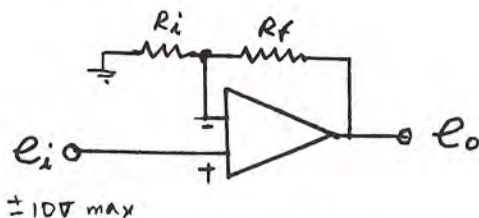

$$e_o = \frac{R_i + R_f}{R_i} e_i$$

This arrangement offer high input impedance with some gain. output is not phase inverted.


High Input Impedance Amplifier

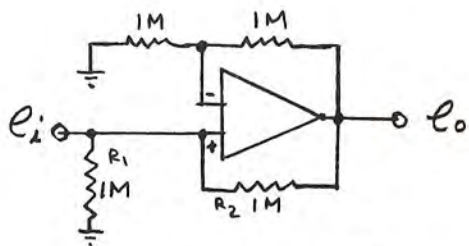

$$e_o = 2 e_i$$


Using positive feedback to input, the input 1 meg resistor may be made to have very high effective resistance.

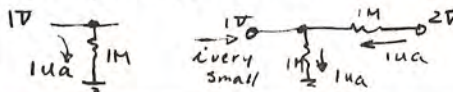For example, if we apply 1 v to R₁ current of 1 ua flow. since amplifier have gain of 2, the output voltage is 2volts. This results current feedback (+) from output to input so that current into R₁ is supplied by amplifier.




NONLINEAR AMPLIFIER (diode)


Simple nonlinear amplifier

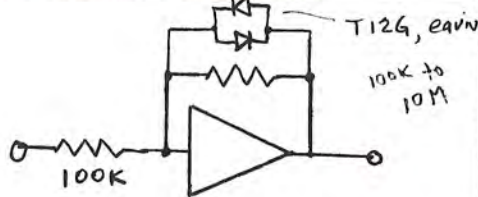

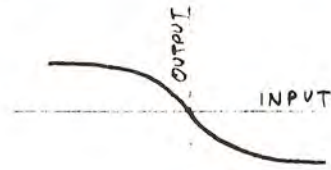If diodes are placed in the feedback circuit, this amplifier acts as compression type amplifier.




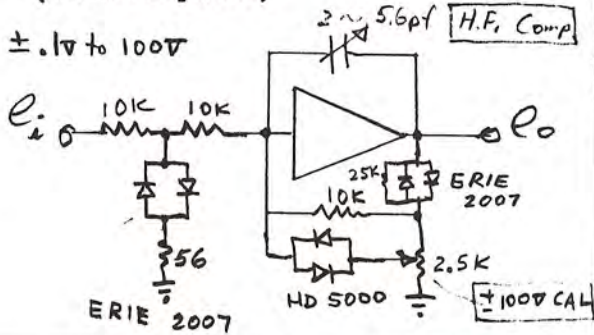Logarithmic type amplifier (fast response)





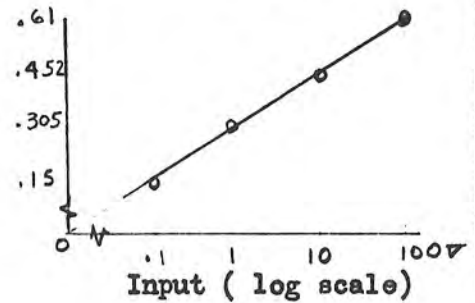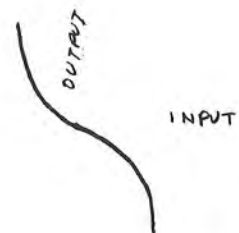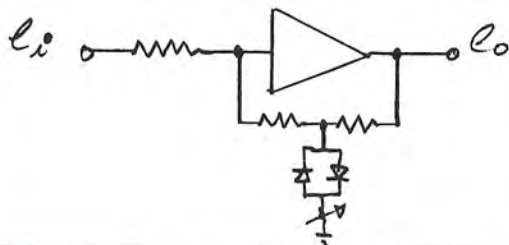
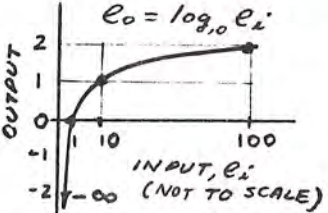
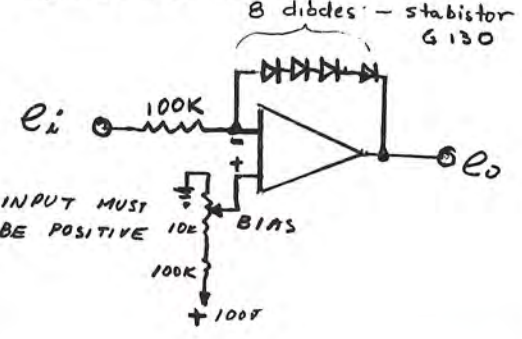
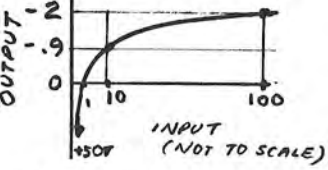
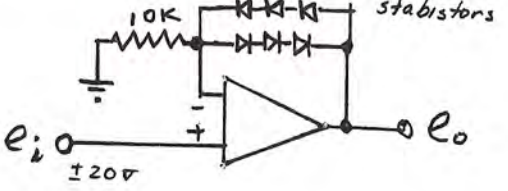

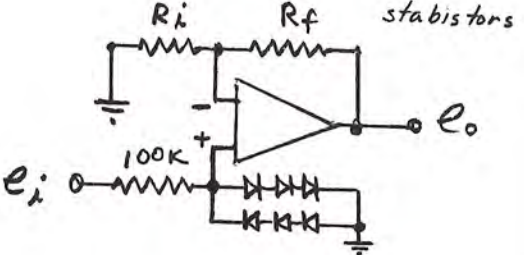
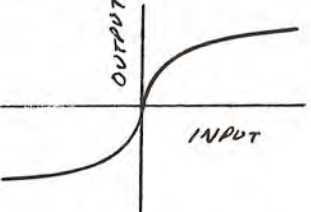
$$e_o \approx .305 + .15 \log_{10} e_i$$

Output



Expansion amplifier




NONLINEAR AMPLIFIERS (log. diode)	CHARACTERISTICS
<p>Theoretical logarithmic amplifier</p>  <p>INPUT MUST BE POSITIVE</p> $e_o = A \log_b e_i$	 <p>An advantage of true log amplifier is capability of accepting wide range of input signal level, Since input can not be negative value, for ac measurement symmetrical amplifier is recommended.</p>
<p>Approximate logarithmic amplifier</p> <p>8 diodes - stabistor G 130</p>  <p>INPUT MUST BE POSITIVE</p>	 <p>Simulating true log amplifier. Bias is adjusted to give zero volt when input is 1-v. when input is zero amplifier saturates to ≈ 50volts. Many germanium diodes can be used such as T 12G. for more dynamic range & controlled characteristics, stabistors are recommended.</p>
<p>Symmetrical nonlinear amplifier</p> 	 <p>Input is limited to 20v, but it will offer high input impedance. Since this amplifier have back to back diode in the feedback, both signal can be applied. low level application</p>
<p>Symmetrical nonlinear amplifier</p> 	 <p>This amplifier also give symmetrical output response with approximate logarithmic compression. For given signal level R_i & R_f may be adjusted for satisfactory out put level.</p>

For temperature stability place diodes in a temperature controlled oven.

NONLINEAR AMPLIFIERS (transistor)

CHARACTERISTICS

Approximate logarithmic

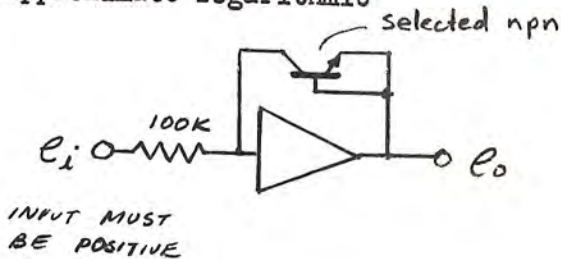


$$e_o \approx -A / \log_b e_i$$

Certain NPN transistor exhibit logarithmic voltage current breakdown characteristics in reverse direction. This arrangement can accept only positive input signal.

Selection of npn transistor may make this type of logarithmic amplifier impractical since use of certain type diodes can give more predictable logarithmic characteristics. (only advantage is high level output)


Symmetrical nonlinear amplifier

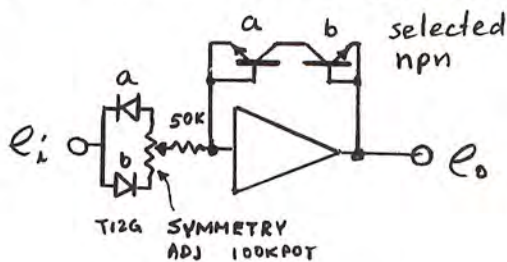


$$e_o \approx -A \log_b |e_i|$$

To accept positive and negative signal two transistors (matched) are used. Limitations are same as listed above.

Symmetrical compressed amplifier

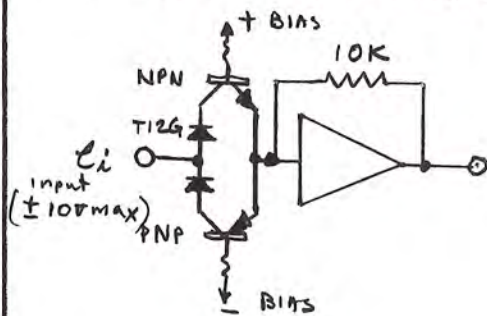


Possible nonlinearity control

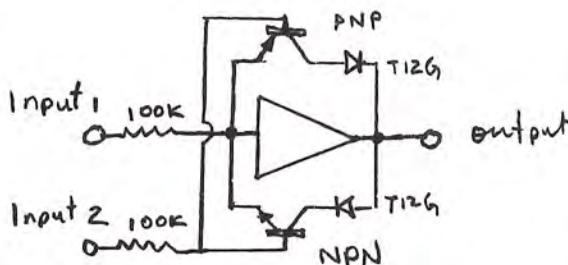


NONLINEAR AMPLIFIER (triodes)

Square Root Amplifier

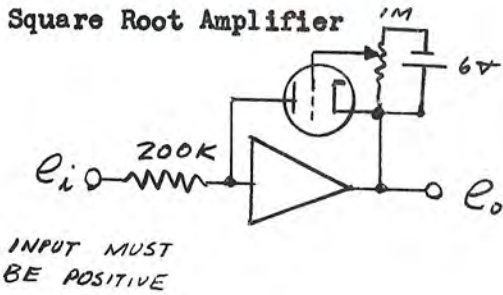


$$e_o \approx -\sqrt{e_i}$$

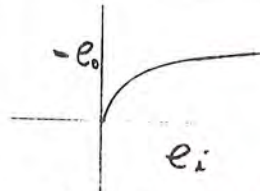


Certain triodes such as 12AU7, muvistor or 7586 may be placed in the feedback circuit to obtain square root characteristics.

Root Function

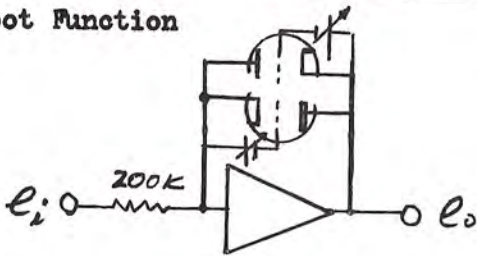


$$e_o = -k|e_i|^{\frac{1}{n}}$$

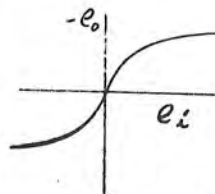


Two triodes placed back to back in the feedback circuit. adjusting bias root may be varied approximately .9 to 10

Power Function

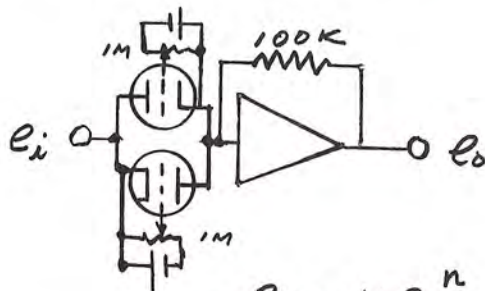


$$e_o = -k e_i^n$$

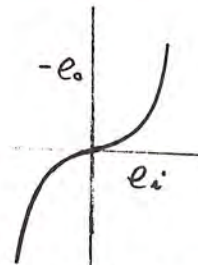


If the triodes are placed in the input circuit, power function may be obtained. the power may be varied .9 to 10 approx.

NONLINEAR AMPLIFIERS (zener diodes)


Limiter Amplifier

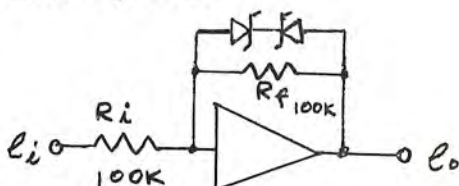

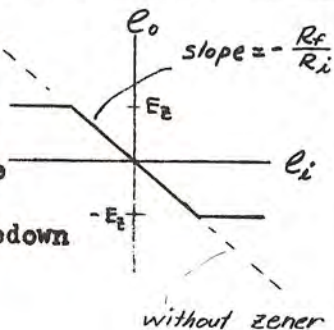
If a back to back zener diode is inserted in the feedback circuit, the output voltage will be limited by the zener breakdown voltage.




Squaring Amplifier

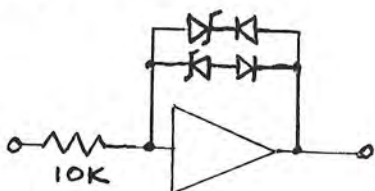

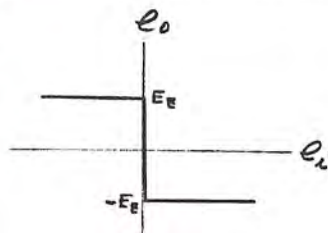
If the feedback resistor in the above amplifier is removed, the amplifier output give very high gain near zero signal. In this arrangement the zener diodes are coupled with low capacity diodes to minimize zener diode capacitance.




Compression Amplifier

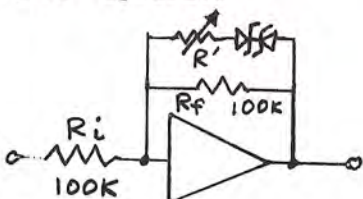

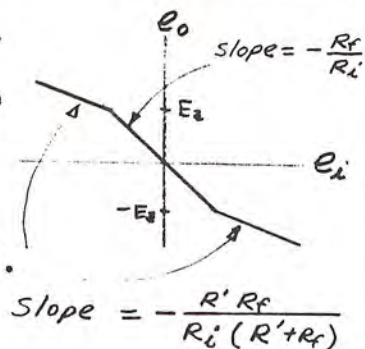
A variable resistor in series with zener diode in the limiter amplifier can control amount of compression for large signal.



Expansion Amplifier

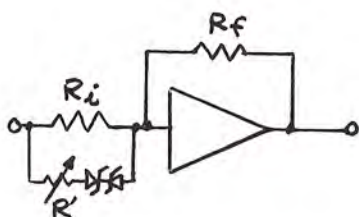

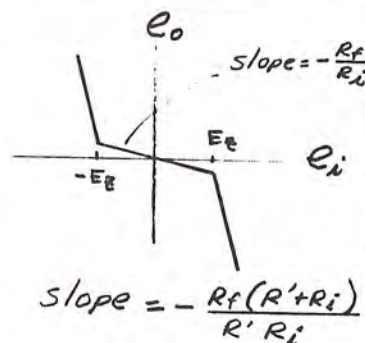
Input output circuit is reversed in this amplifier to obtain higher gain for large signal input




NONLINEAR AMPLIFIERS (zener diode)

simulating nonlinear characteristics


Dead zone

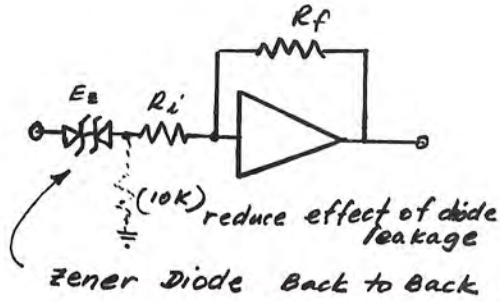



Simulating a dead zone

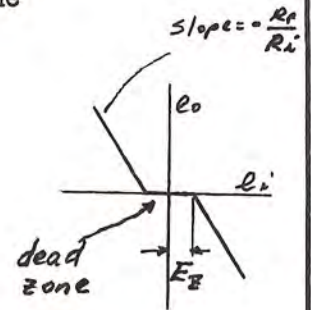


Back-lash

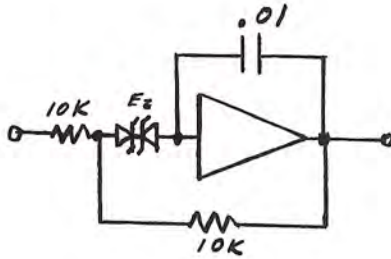

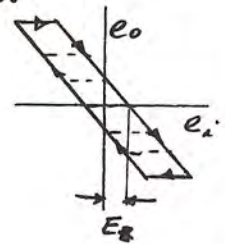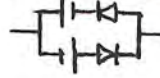
Simulation of backlash; the capacitor hold the voltage and the zener diode conduct voltage across diode exceed brakedown voltage. small battery and low leakage diodes may be replaced for zener for low leakage memory.















Relay

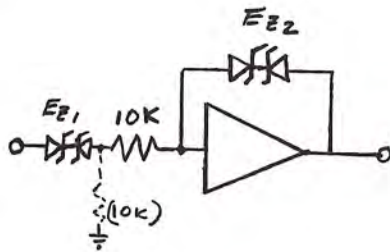

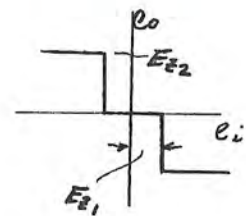Representation of polarized double throw relay which has equal pull-in and pull-out current



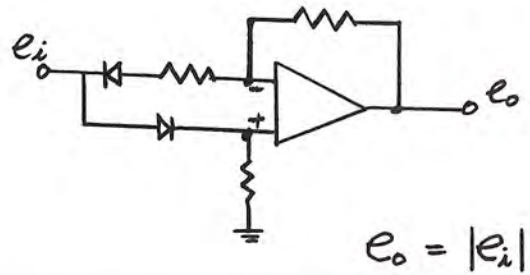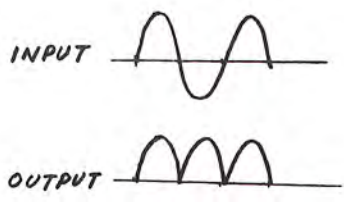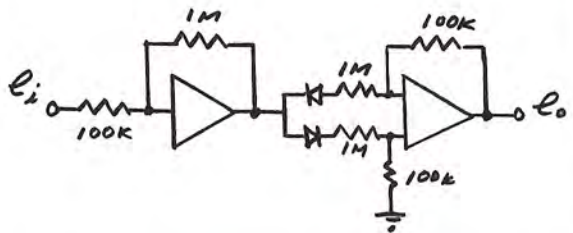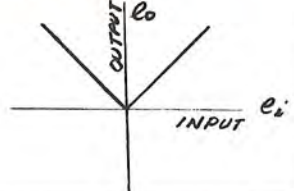
<p>ABSOLUTE VALUE AMPLIFIER</p>	
<p>Full-wave rectification</p>  <p style="text-align: center;">$e_o = e_i$</p>	<p>Output gives full-wave rectified wave of input. Output is always positive sign. Diodes contribute $\approx .3$ voltage drop.</p> 
<p>Full-wave rectification (low level)</p> 	<p>Inserting an amplifier ahead of full-wave rectifier, effect of diode voltage drop is reduced by factor of amplification. This technique may be applied to low level full-wave rectification.</p> 

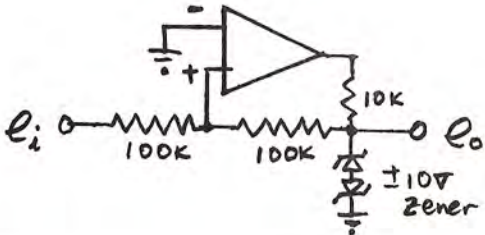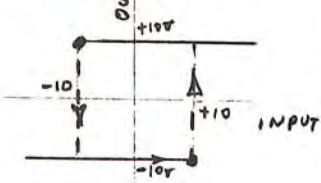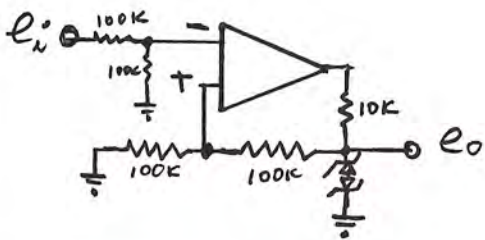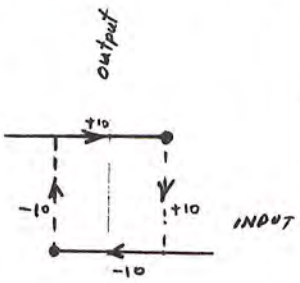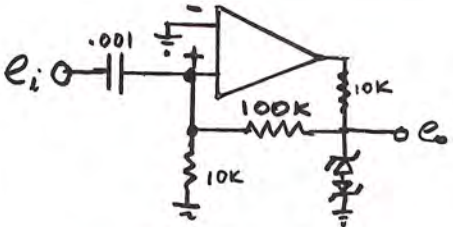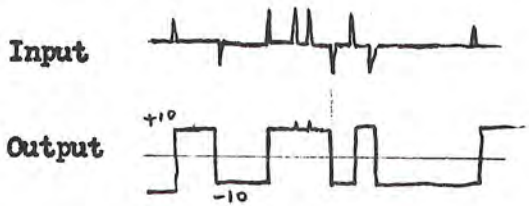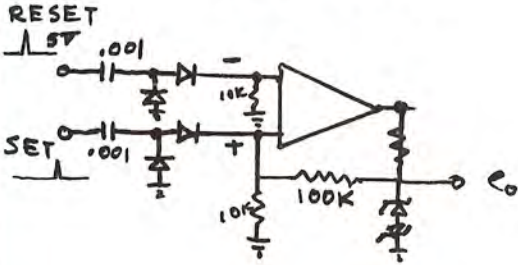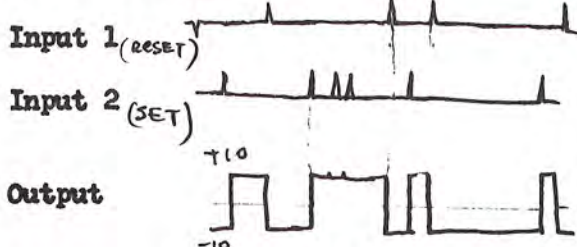
SWITCHING AMPLIFIER (BISTABLE)	CHARACTERISTICS
<p data-bbox="235 296 542 327">Bistable Comparator</p> 	<p data-bbox="824 308 1500 470">Bistable Comparator incorporate a zener diode as a reference, input voltage is compared against reference diode; when input voltage become equal to zener voltage output will flip to ± 10 v.</p> 
<p data-bbox="230 741 534 772">Bistable Comparator</p> 	<p data-bbox="837 753 1451 821">Similar to above, but output will flip to opposite polarity</p> 
<p data-bbox="237 1167 667 1234">Bistable Multivibrator (single input)</p> 	<p data-bbox="833 1171 1446 1293">Out put flip to ± 10v anytime opposite polarity pulse arrives. Once flipped additional pulse of same polarity have no effect</p> 
<p data-bbox="245 1587 630 1654">Bistable Multivibrator (two inputs)</p> 	<p data-bbox="849 1625 1354 1692">AC (pulse) toggle switch action can be obtained.</p> 

DIGITAL TECHNIQUES

Pulse-Height to Time converter

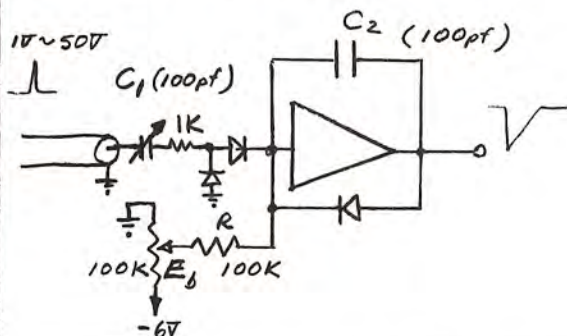


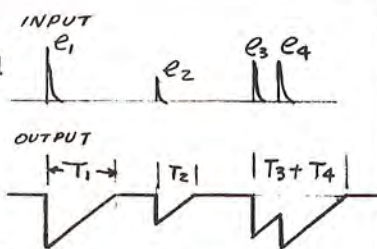If a positive pulse is applied to the input, it will charge C_1 and this charge is also damped into C_2 , causing the output to step down. This voltage is discharged by integrator




$$T \approx \frac{RC_1}{E_b} e_{pulse}$$

Time to Voltage Converter

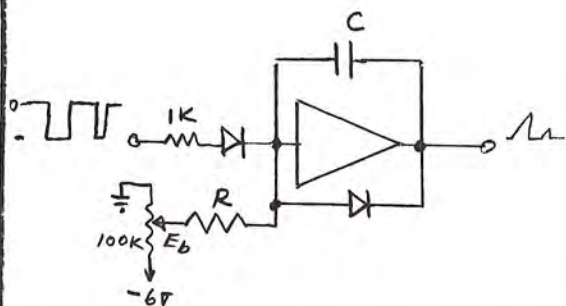


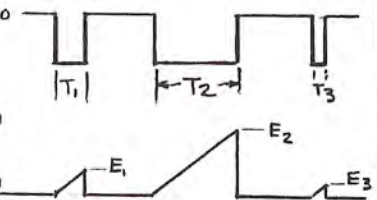A negative gate opens the diode gate allow the integrator to integrate at the constant rate. The peak voltage is thus proportional to the time (period).




$$E \approx \frac{E_b}{RC} T$$

DC Voltage to Frequency Converter

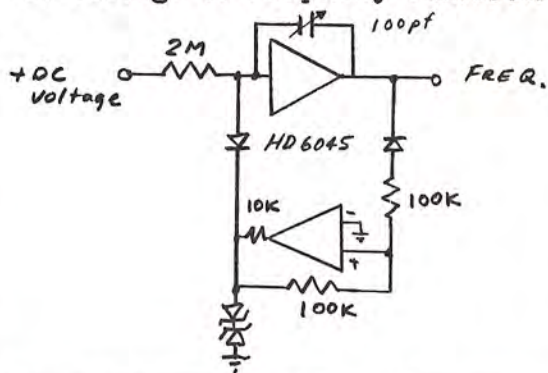


This will give conversion factor of approximately 1 kc per 10 volts input.

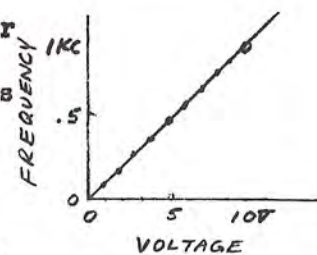The conversion accuracy is in the neighborhood of $\pm 1\%$.



Binary to voltage converter


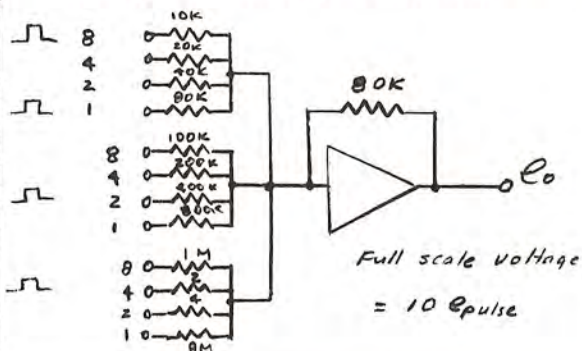


Simple Binary (BOD) to voltage conversion is accomplished by summing input pulse voltages through the properly weighed input resistors.

If input pulse has - 1 volt, the full scale voltage will be 9.99 volts.



PEAK MEMORY AMPLIFIERS

Peak memory amp

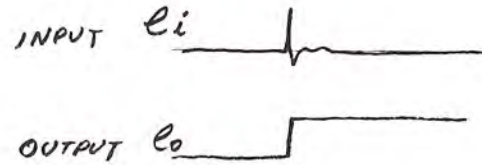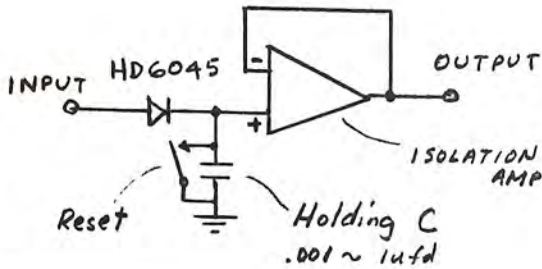


The holding capacitor is charged through low leakage diode, since the leakage of diode (1 nanoamp) and grid current (.5 nanoamp) are low, voltage can be held

Fast response peak memory amp

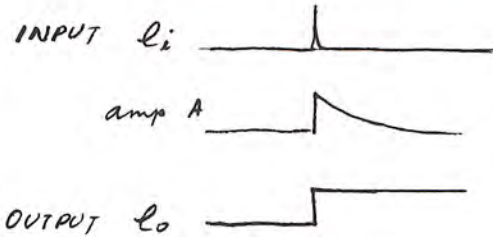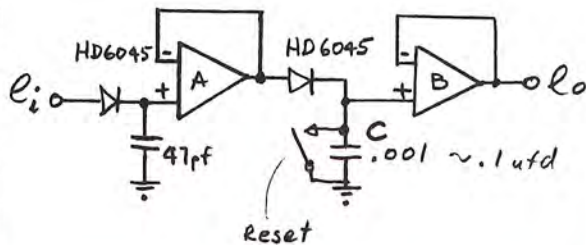

To reduce input loading effect, two amplifiers may be cascaded


Integrator peak memory

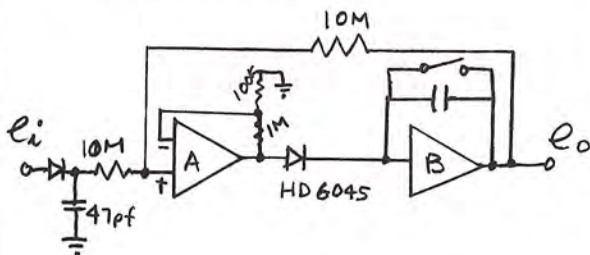

Integrator is used as memory to improve dc accuracy.

SAMPLE-HOLD AMPLIFIER

Sample hold

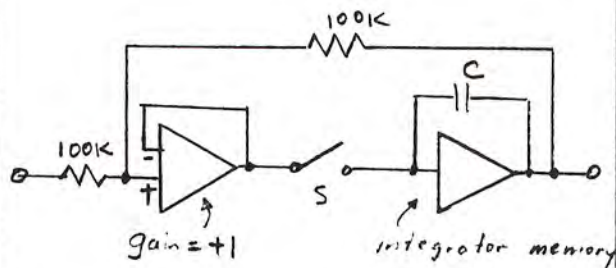


S - SWITCH momentary close to sample


(Illustration of sample hold circuit.)

This circuit is often called integrator memory: When the switch is closed the capacitor is charged by the first amplifier. When the switch opens the integrator holds the voltage until the switch is closed again.


Sample Hold amplifier

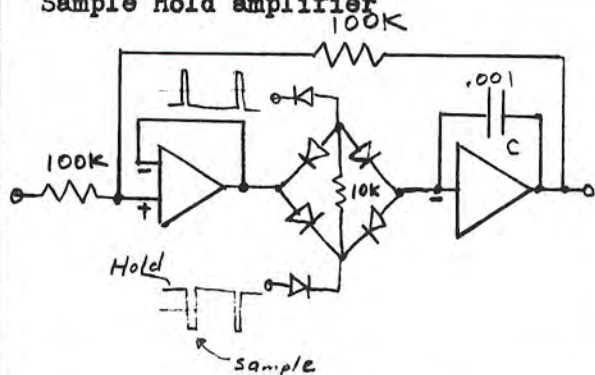

Input

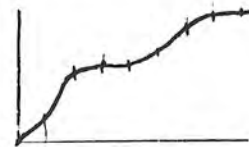

Sample command pulse

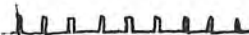


output



SAMPLED-DATA


Sampling Integration

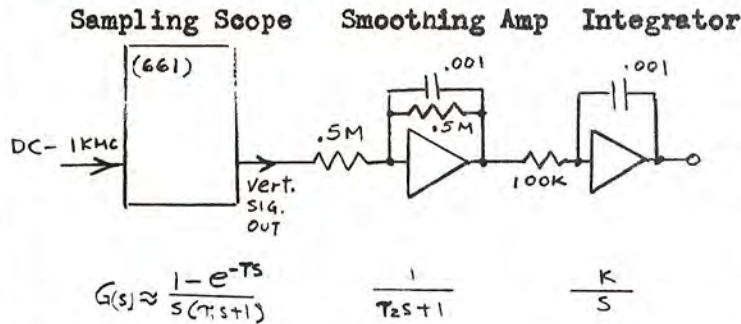

Sampled-data contain many higher frequency components as well as desired lower Frequency signals.


In many operation, it may be necessary to insert a smoothing amplifier before doing a linear operation. It is possible to integrate repetitive signal to approximately 1 kmc using sampling scope vertical signal out.

Sampled-pulse Integration

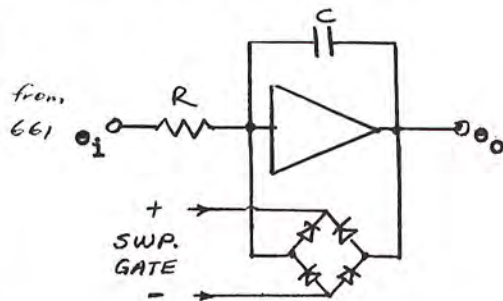


Sampled-pulse may be integrated to obtain area of the pulse in volt sec. Proper scaling factor to convert real time to sampling time is necessary.

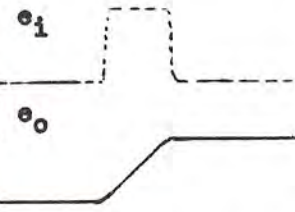Detail of gating circuit see gated integrator.




Sampled-pulse Differentiation

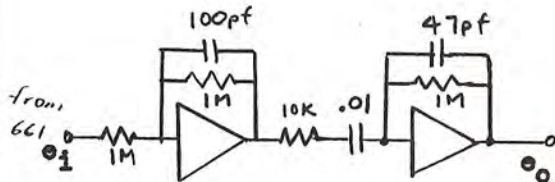


Differentiation of sampled pulse may be performed after passing the sampled signal through a smoothing amplifier.

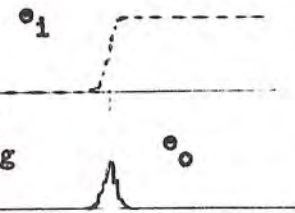
Additional H.F. limiting circuit is necessary in differentiation.



Possible risetime compensation circuit

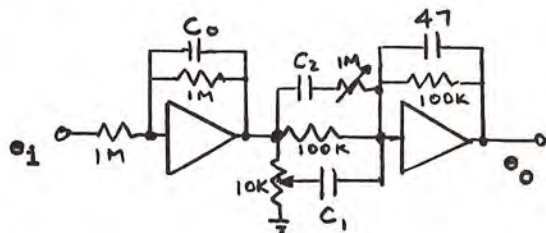


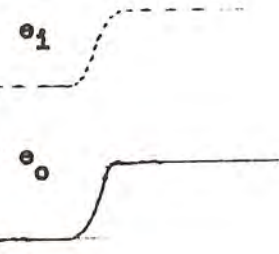This arrangement can provide possible risetime improvement, however this type of compensation is applicable to a given frequency and given sweep speed.




L. F. FUNCTION GENERATORS

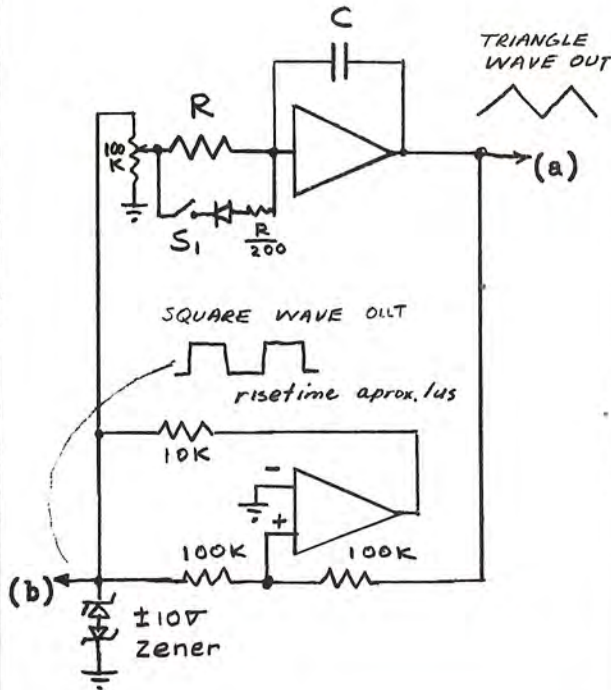Triangle, Square, Sawtooth & Pulse Generator




Combining an integrator and a bistable comparator, precise low frequency waveforms can be generated. Operational amplifier B is working as a bistable comparator which switches when input reach + or - 10 volts and output puts out ± 10 volts square wave.


Normal waveform at (a) and (b) are

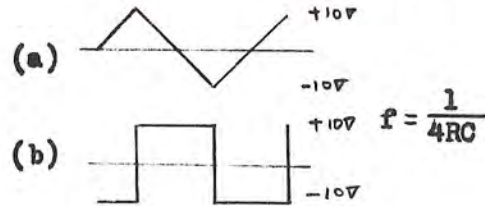


When switch S_1 is closed,

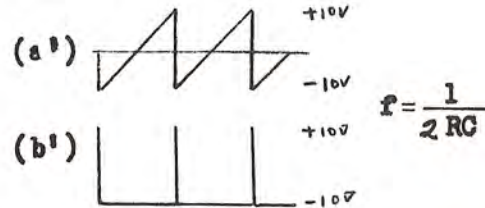

L.F. Sine Generator

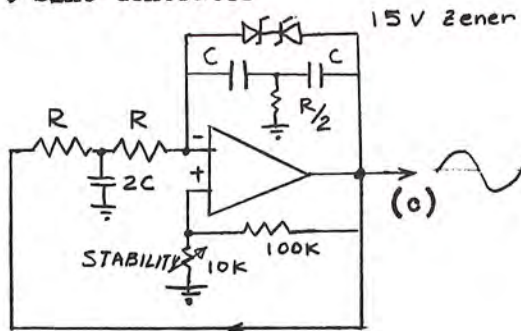


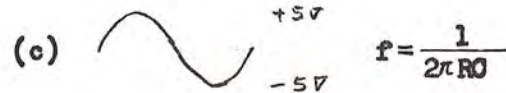A very low frequency sine wave can be generated with twin T filter network in the feedback loop of a operational amplifier. Positive feedback is provided to sustain oscillation. Amplitude is controlled by a nonlinear impedance of zener diode in the negative feedback.




CRT FUNCTION GENERATOR

Simple System

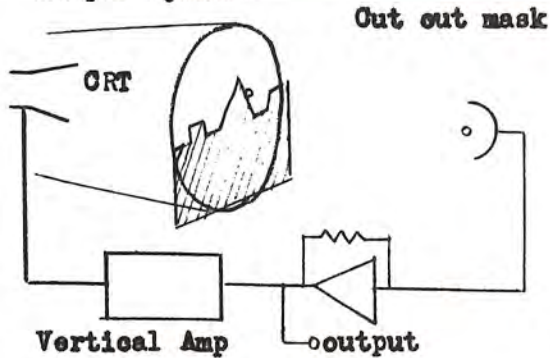

A light sensitive element is placed in front of the CRT and the mask. If the beam is above the mask, negative signal will be produced to force the beam to move down. Normally the beam is positioned above the mask so that beam always tries to go up, however, the light feedback does not allow the beam to show too much. As a result the beam follows the cut out mask. DC coupled signal can be obtained at the output of operational amplifier.

Differential Fast System

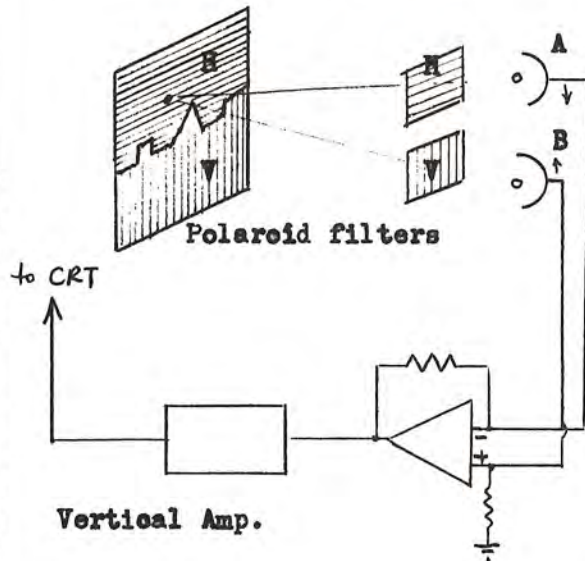


When using the simple system the spot size has to be made small to obtain good resolution, but when it is operated at the low light level it will suffer from speed.

The differential system incorporates polaroid filter masks and two light sensing elements. Substantial improvement in speed and resolution may be expected.

When the beam spot is in H plane the light is sensed by light sensor A. B will not receive light since the filter is out of phase. Thus the signal from A will force the beam to move down. If the beam spot is in V plane it, likewise, will be forced upward by B.

The light is picked up differentially and the beam is moved push-pull action.

Mask Cutting


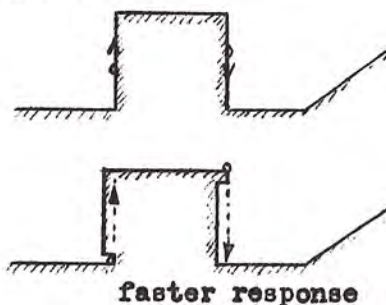


The mask can be undercut to improve response time.

The polaroid filter may be cut by using a hot resistance wire; the temperature can be adjusted by controlling current.

SEGMENTS FUNCTION GENERATOR

Segments function generator

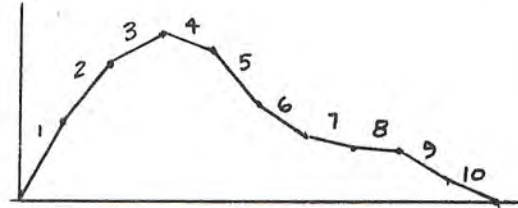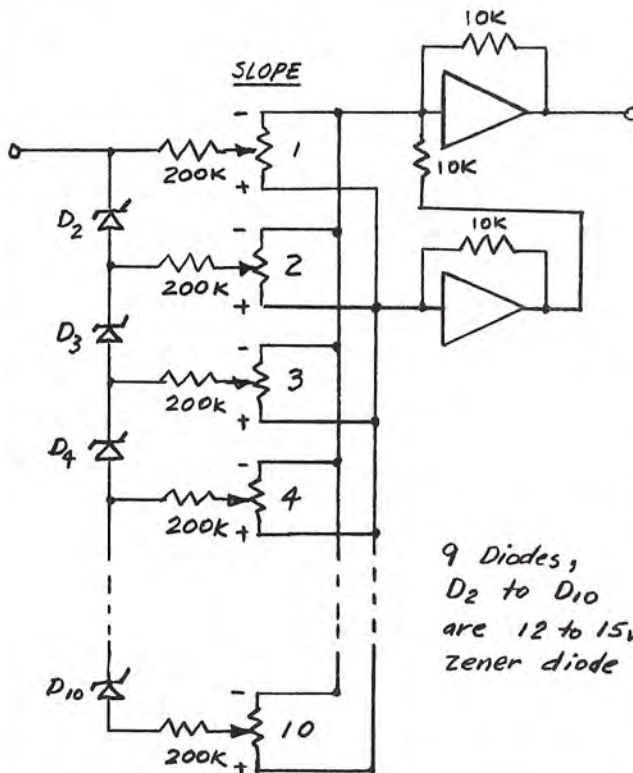

Straight line approximated function can be generated with the aid of zener diodes and potentiometer.



Zener diodes are normally cut-off. As sawtooth is applied zener diodes start conducting with some voltage intervals, thus making a line brake points.

Slope of each segment is adjusted by the potentiometers.

Note that no external voltages are required.

B - H LOOP PLOTTING

B-H Curve Plotting

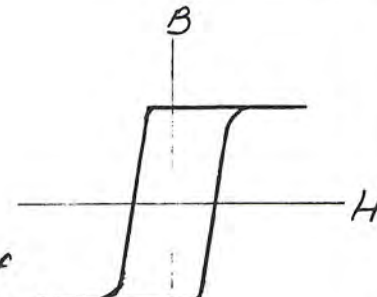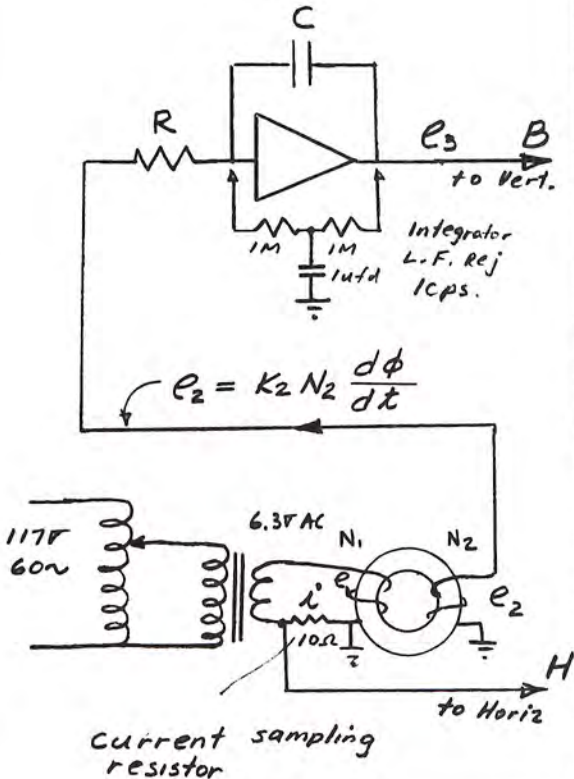

The voltage of the secondary, e_2 , is given

$$e_2 = K_2 N_2 \frac{d\phi}{dt}$$

If we integrate e_2 , the output of integrator e_0 will be proportional to flux ϕ ,

$$e_0 = -\frac{1}{RC} \int K_2 N_2 \frac{d\phi}{dt} dt = -\frac{K_2 N_2}{RC} \phi$$

Since $B = \phi/A$


$$B = -\frac{RC}{K_2 N_2 A} e_0 \quad \leftarrow$$

H is given

$$H = \frac{K_1 N_1}{l} i \quad \leftarrow$$

CAPACITY MEASUREMENT (1 pf 10 ufd)

Basic idea

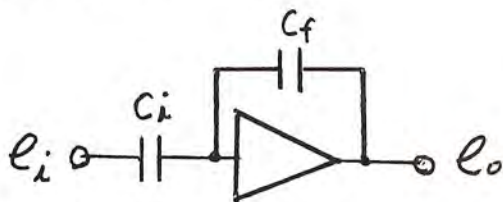


$$e_o = - \frac{C_i}{C_f} e_i$$

When capacitors are placed in input- and feedback, it will make an amplifier. Gain of this amplifier is $-C_i/C_f$, ratio of input C to the feedback C. Since the output voltage of the amplifier is proportional to the C_i , it is possible to measure capacitance.

Theoretically, this amplifier should have ∞ response but drift and leakage limits the low frequency response.

For high frequency, charging current limits the response - smaller C be used.

Capacity 100pf ~ 1uf

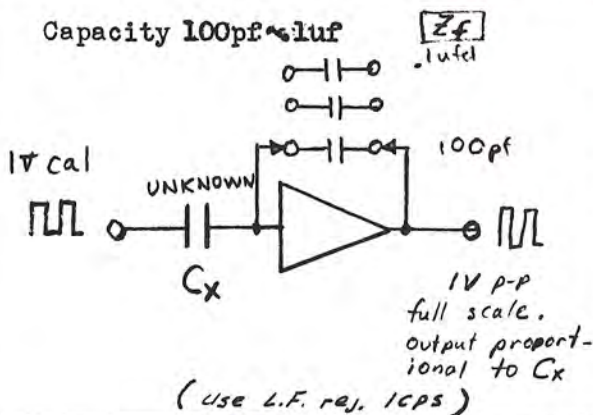


Unknown capacitor is compared to the precision internal feedback capacitor. When unknown C is same as feedback C the output voltage is 1 volt and it is directly proportional to C.

The output voltage can be monitored by scope or meter.

The calibrator impedance is too high to drive higher capacitance therefore, use of isolation amplifier is recommended as shown below.

(use integrator L.F. rej. at 1cps.)

Widerange Capacity Meter
1pf to 10uf

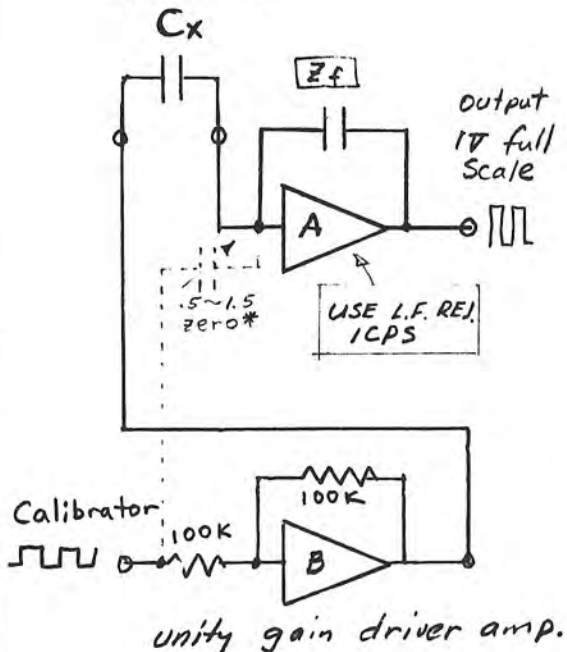


Careful arrangement enable capacitance measurement for value 1pf to 10uf.

RANGE	Cal.	Z _f
0 - 10uf	10mv	.1
0 - 1uf	.1v	.1
0 - .1	.1v	.01
0 - .01	.1v	.001
0 - .001	1v	.001
0 - 100pf	10v	.001
0 - 10pf*	10v	.0001

* to compensate stray capacity, adjust neutralizing c for zero c.


RISETIME BEAM INTENSIFIER

Risetime intensifier

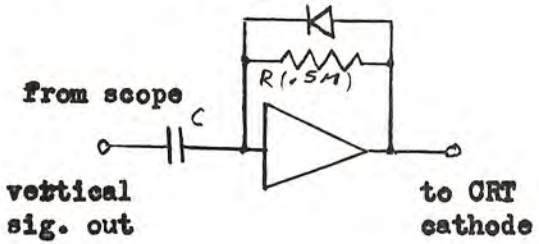


A differentiator can be used as a beam intensifier in certain experimental set up. Scope vertical signal out can provide signal to the differentiator and the output is fed to the CRT cathode. A word of caution, vert. signal output should not be monitored by the same scope. possible oscilation may result.


Rise & Fall time intensifier

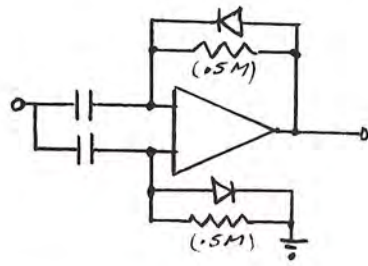

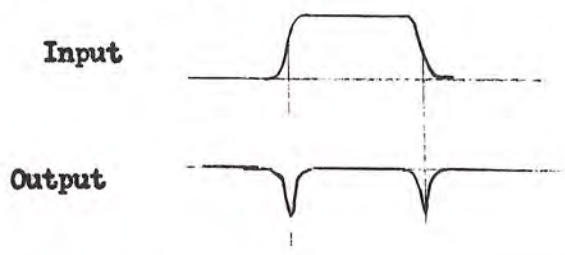
Appling signal to the both positive and negative grid, both rise and fall time can be intensified



Intensity control


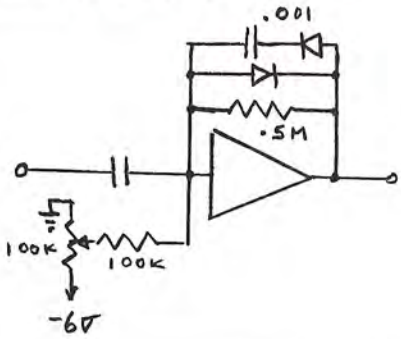


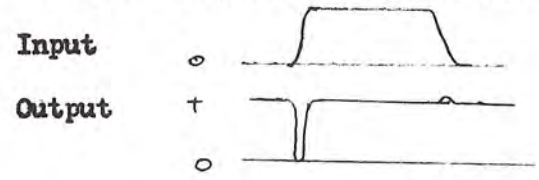If the cathode is over drived a serious defocusing may result thus some means of maximum intensity limiter is disiered. In this circuit biased diodes limit the output swing to privent defocusing.





VELOCITY ACCELERATION STUDIES

Velocity plot

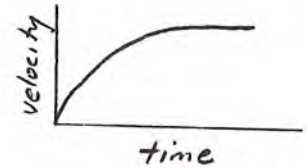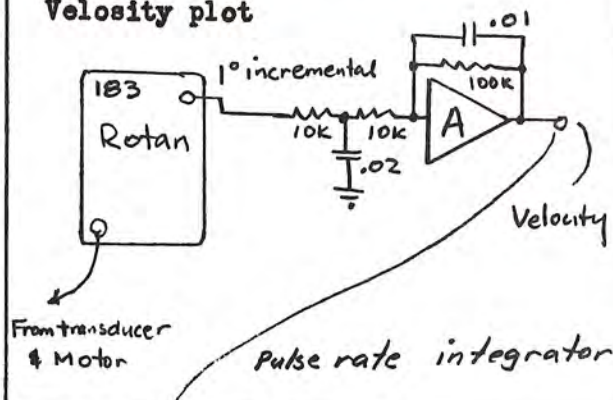

Rotational velocity may be obtained by integrating pulse rate, using the ROTAN 1° incremental pulse


Acceleration plot

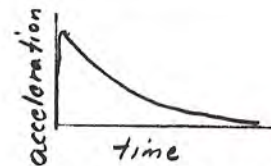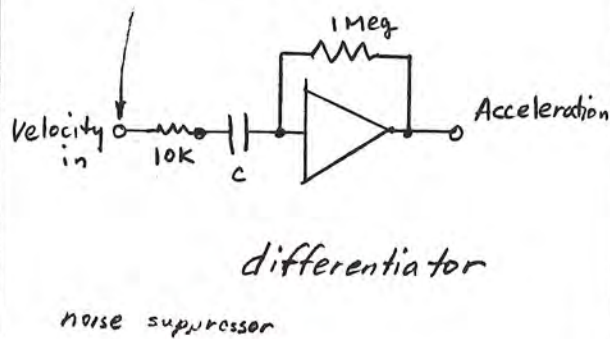

Velocity signal is differentiated to obtain acceleration. 10k resistor is added to suppress noise.


Speed - Torque Plot

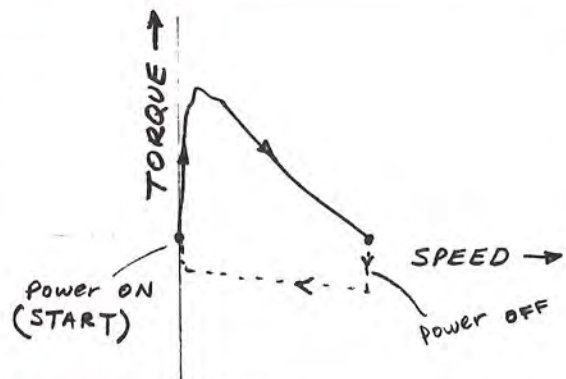X Y plot of velocity & acceleration gives a speed - torque plot. A typical motor characteristics may be obtained by starting and stopping the motor and observing the torque speed characteristics.




TRANSFER FUNCTIONS, e_o/e_i

$G(s) = -k$

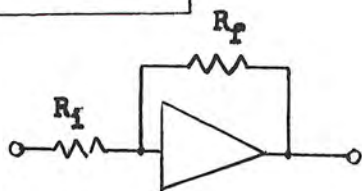


$k = \frac{R_F}{R_1}$

$G(s) = K(Ts - 1)$

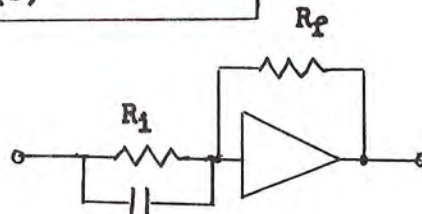


$k = \frac{R_F}{R_1} \quad T = R_1 C$

$G(s) = -\frac{k}{s}$

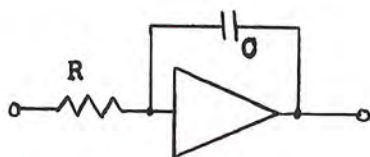


$k = \frac{1}{RC}$

$G(s) = -\frac{k}{s(Ts - 1)}$

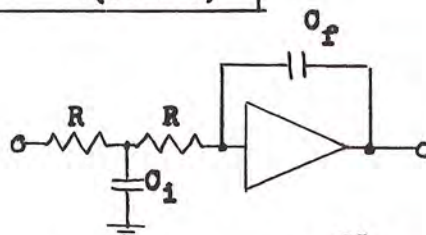


$k = 2RC \quad T = \frac{RC_1}{2}$

$G(s) = -ks$

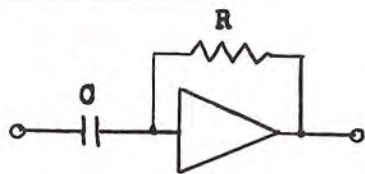


$k = RC$

$G(s) = \frac{-1}{4T^2 s^2}$

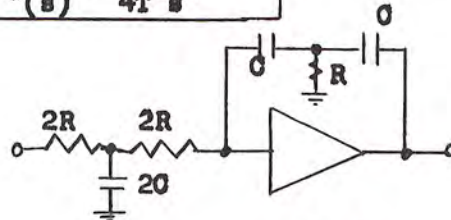


$T = RC$

$G(s) = \frac{-k}{(Ts - 1)}$

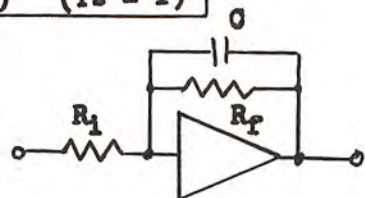

$k = \frac{R_F}{R_1} \quad T = R_F C$

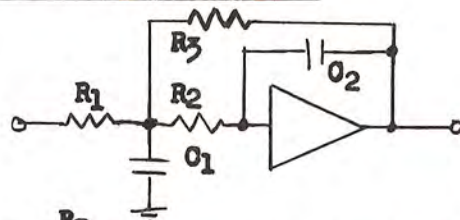
$G(s) = \frac{-k_1}{k_2 s^2 + k_3 s + 1}$




$k_1 = \frac{R_3}{R_1}, \quad k_2 = R_2 R_3 C_1 C_2, \quad k_3 = \frac{(R_2 R_1 + R_3 + R_2) C_2}{R_1}$

TUNNEL DIODE STUDIES

Tunnel Diode Stability

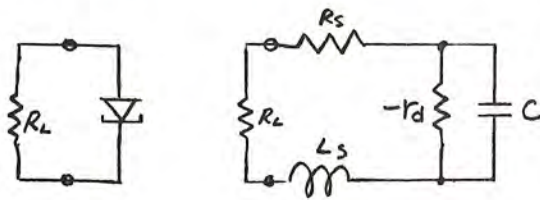


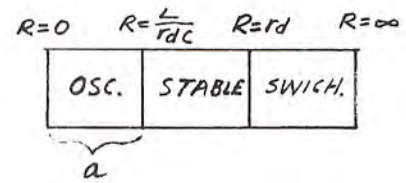Tunnel diode stability criteria is given ■




a. (can be made conditionally stable at low frequency)

Tunnel Diode E-I curve

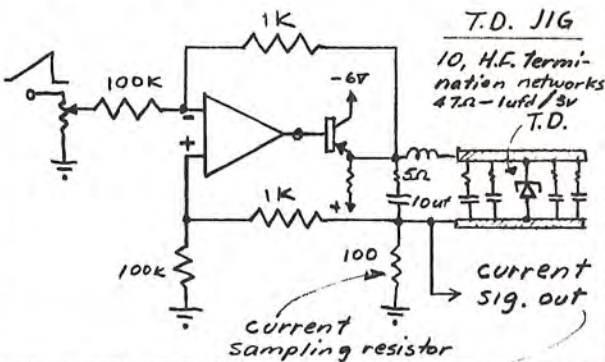


Operational amplifier with additional E.F. can drive tunnel diode with very low impedance.

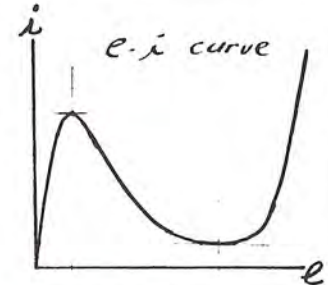
T.D. jig stabilizes diode at High frequency. Thus tunnel diode may be driven by very slow ramp.



Tunnel Diode di/de curve

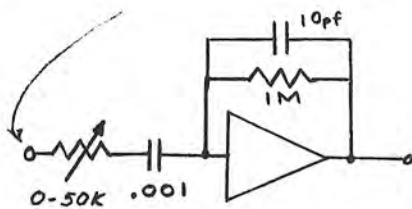

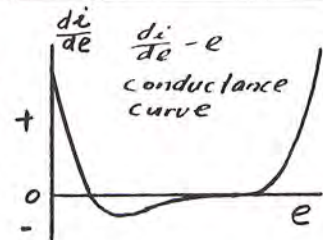Linear drive of tunnel diode allow differentiation of current to obtain di/de curve



Tunnel diode quantum phenomenon may be observed at very low temperature.


Some tunnel diodes in liquid Helium indicate wiggles on the conductance curve.



* detail discussion of stability refer to "Some notes and applications on tunnel diodes" by Jaek Rogers, Tektronix, Inc. , February, 1961

TUNNEL DIODE STUDIES, Risetime characteristics


Tunnel Diode Switching

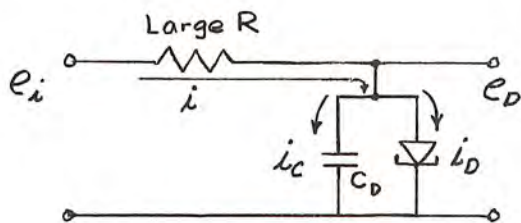

$C_D =$ Equivalent diode capacity


Assumptions:

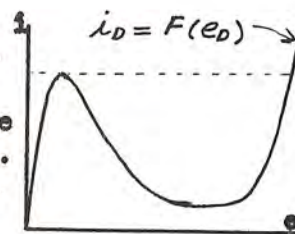- 1) Leads inductance negligible.
- 2) Diode capacitance assumed constant.
- 3) Constant current applied to the diode.



$i =$ applied current, $i_D =$ diode current
 $i_c =$ current to charge diode capacity

Block Diagram

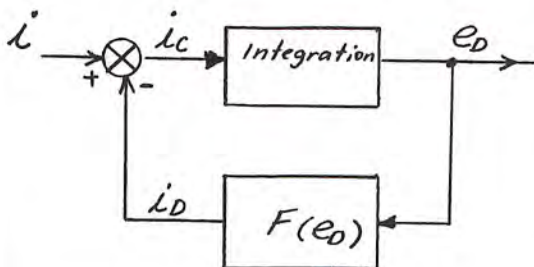

Summing all the current at the node of e_D , we have

$$i - i_c - i_D = 0 \quad \dots \dots 1$$

$$i_c = i - i_D \quad \dots \dots 1a$$

$$i = \frac{e_i - e_D}{R} \quad \dots \dots 2$$

$$i_c = C_D \int \frac{de_D}{dt} \quad \dots \dots 3$$

$$i_D = F(e_D) \quad \dots \dots 4$$

Integrating (3)



$$e_D = \frac{1}{C_D} \int i_c dt \quad \dots \dots 5$$

Substituting eq. (1a)

$$e_D = \frac{1}{C_D} \int (i - i_D) dt \quad \dots \dots 5a$$

The equation (4) and (5a) are represented by the block diagram, and operational amplifier circuit is shown at left.

Analog Solution of Risetime*

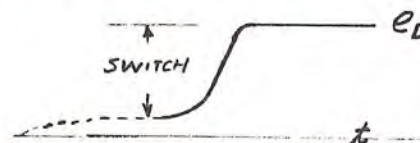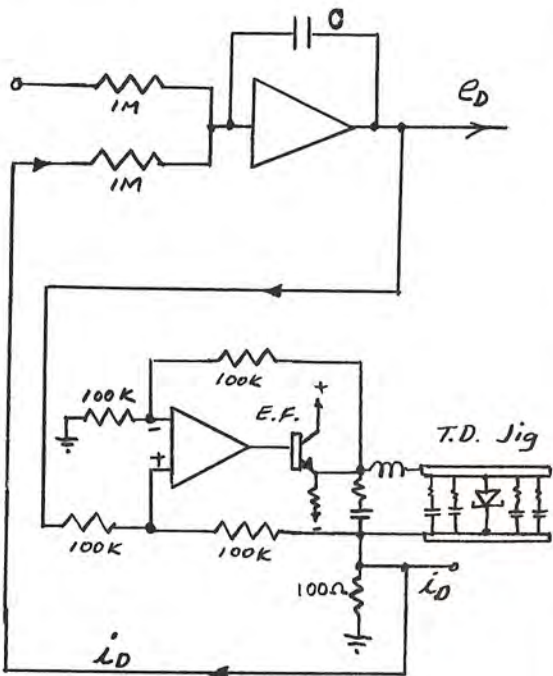

If the integrating capacitor C is chosen $0.01 \mu\text{fd}$ for diode capacitance, C_D , 1 pF ; the scaling factor will be 1 nsec real time equal to 10 msec analog time.

* It is possible to compute diode capacitance from diode switching time.

